
Hardware Queues

Eylon Caspi
University of California, Berkeley
`eylon@cs.berkeley.edu`

4/8/05


Outline

- ◆ **Why Queues?**
- ◆ **Queue Connected Systems**
 - “Streaming Systems”
- ◆ **Queue Implementations**
- ◆ **Stream Enabled Pipelining**


Modular System Design

- ◆ **Decompose into modules to manage complexity, performance**
- ◆ **How to connect modules?**


- Wires

 


- Shared bus

 

- Register File / Memory

 


- Point to pt. channels

 

Flow Control


- ◆ **Synchronous operation**

- Data every cycle

 


- ◆ **Producer may stall**

- Data **valid** signal

 


- ◆ **Consumer may stall**

- **Back-pressure** signal

 


- ◆ **Either may stall**


- **Valid** + **Back-pressure**

 

Example: Bursty Communication

 


 - ◆ **Producer envelope:** (8 cycles)
- ◆ **Consumer envelope:** (8 cycles)
- ◆ **Together:** (11 cycles)




- ◆ **Bursty communication**
 - P + C each have average throughput 1/2
 - Producer is bursty
 - Consumer is steady

Bursty Communication + Queue

 

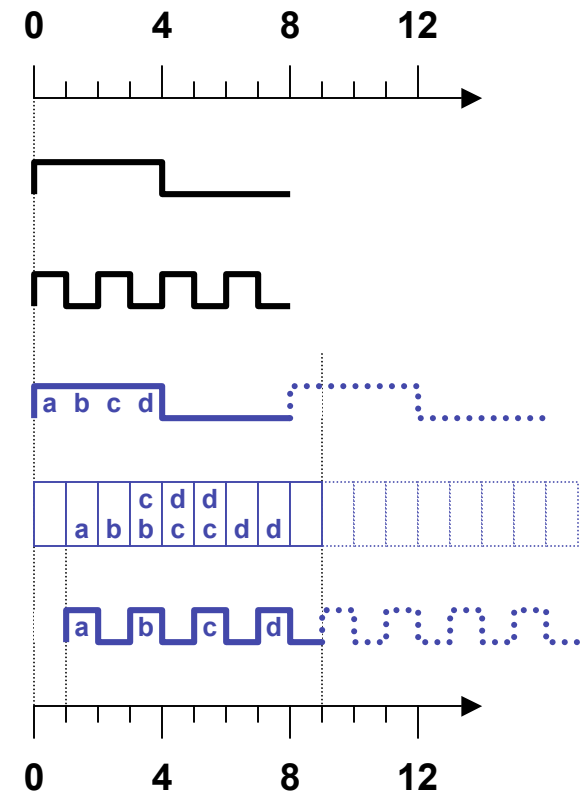- ◆ **Producer envelope:** (8 cycles)
- ◆ **Consumer envelope:** (8 cycles)
- ◆ **Producer \rightarrow Queue:** (8 cycles)
- ◆ **Queue contents:**
- ◆ **Queue \rightarrow Consumer:** (8 cycles)




Abstract Queue

◆ Container that maintains order

- FIFO = First In, First Out
- Maintains system correctness regardless of communication delay

◆ 4 interfaces (methods)

- Full, Empty, Put, Get

 


Queues Reschedule Data

◆ For performance


- Smooth bursty communication
- Smooth dynamic rate communication

◆ For correctness – prevent deadlock

 - Align data tuples that arrive with different delays, like pipeline registers



 - Reorder: $P:\{x,y\}$ $C:\{y,x\}$
- Store: $P:\{x^*,y\}$ $C:\{x,y\}$



◆ For convenience



- Buffer up / packetize to communicate with microprocessor
- Off chip
- Time multiplexed computation (SCORE)

Streaming Systems

- ◆ **Suppose queues were the *only* form of IPC**
 - *Stream* = FIFO channel with buffering (queue)
 - Every compute module (*process*) must stall waiting for
 - ◆ Input data
 - ◆ Output buffer space
- ◆ **System is robust to delay, easy to pipeline**
- ◆ **Hardware design decisions:**
 - Stream / flow control protocol
 - Process control (fire, stall)
 - Queue implementation
 - Stream pipelining
 - Queue depths

Wire Protocol for Streams

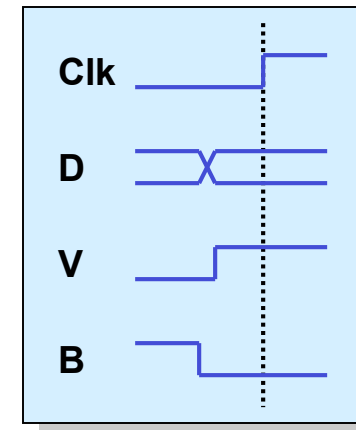 - ◆ **D = Data, V = Valid, B = Back-pressure**
- ◆ **Synchronous (rendezvous) transaction protocol**
 - Producer asserts **V** when **D** ready, Consumer deasserts **B** when ready
 - Transaction commits if $(\neg \mathbf{B} \wedge \mathbf{V})$ at clock edge




Process Control (Fire / Stall)

◆ In state X, *fire* if

- Inputs desired by X are ready (Valid)
- Outputs emitted by X are ready (Back-pressure)

◆ Firing guard / control flow
 
```
if (iv && !ob) begin
    ib=0; ov=1;
    ...
end
```




◆ Subtlety: master, slave

- Process is slave
 - ◆ To synchronize streams, (1) wait for flow control in, (2) fire / emit out
- Connecting two slaves would deadlock
- Need master (queue) between every pair of modules

Queue Implementations


◆ Systolic

- Cascade of depth-1 stages (or depth-N)

 


◆ Shift register

 - Put: shift all entries
- Get: tail pointer




◆ Circular buffer

- Memory with head / tail pointers

 


Enabled Register Queue

- ◆ **Systolic, depth-1 stage**
- ◆ **1 state bit (empty/full) = V**
- ◆ **Shift data in unless**
 - Full and downstream not ready to consume queued element
- ◆ **Area → 1 FF per data bit**
- **Area on FPGA**
 - Area → 1 LUT-FF cell per data bit
 - 🕒 But depth-1 (1 stage) is nearly free, since data registers pack with logic
- ◆ **Speed: as fast as FF**
 - But combinational connects producer, consumer, via B

 


Xilinx SRL16

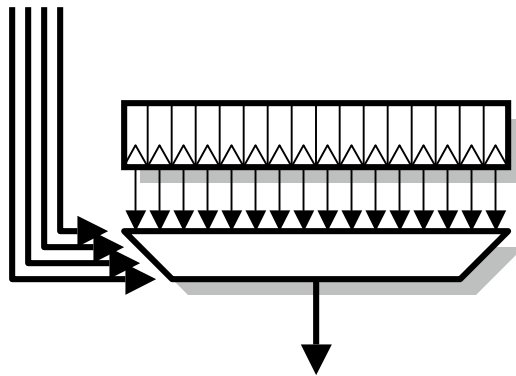- ◆ **SRL16 = Shift register of depth 16 in one 4-LUT cell**
 - Shift register of arbitrary width: *parallel* SRL16, arbitrary depth: *cascade* SRL16
- ◆ **Improve queue density by 16x**




4-LUT Mode

 

SRL16 Mode

Shift Register Queue

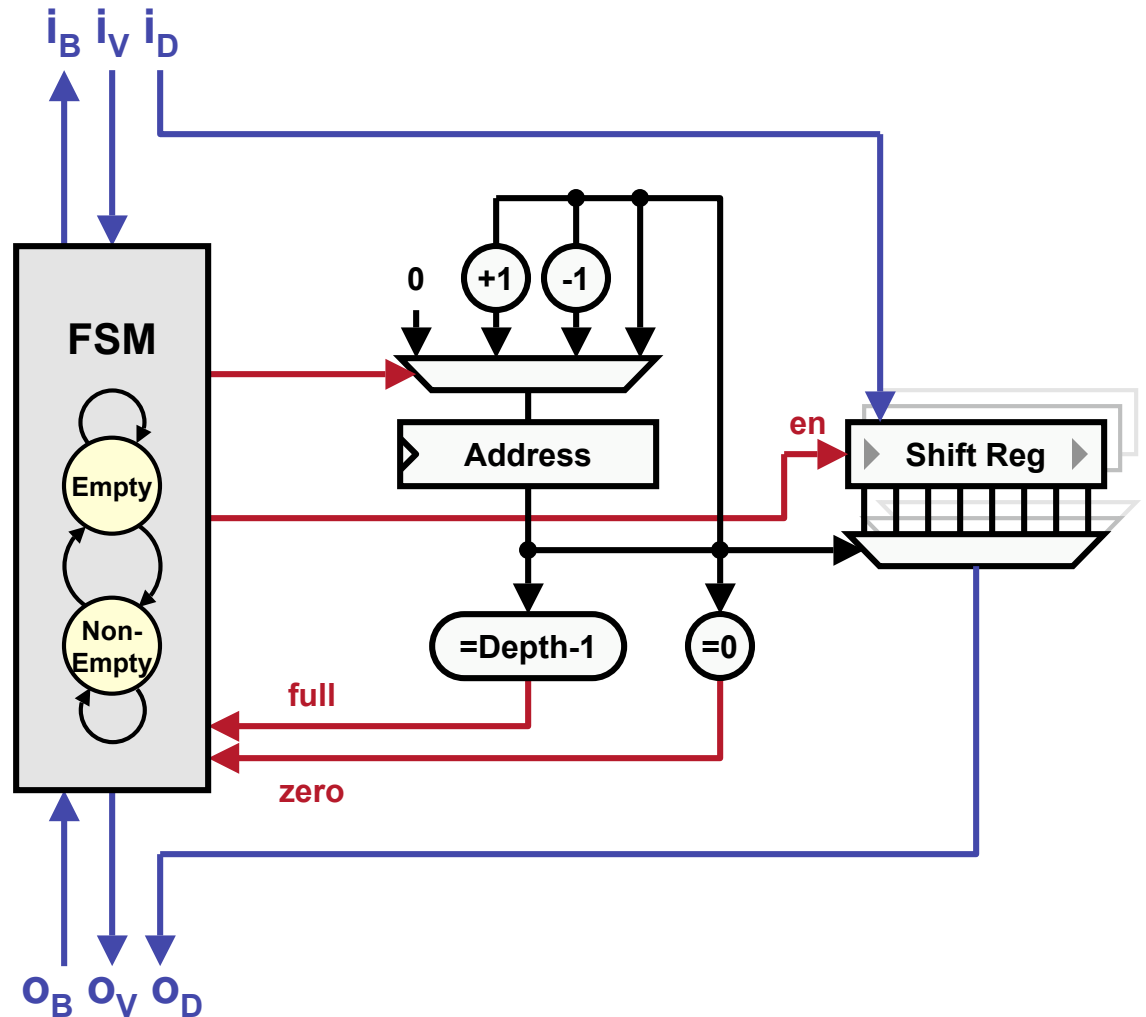- ◆ **State: empty bit + capacity counter**
- ◆ **Data stored in shift reg**
 - In at position 0
 - Out at position *Address*
- ◆ **Address = number of stored elements minus 1**
- ◆ **Flow control**
 - $o_v = (State == Non-Empty)$
 - $i_b = (Address == Depth-1)$
- ◆ **FSM decides**
 - Whether to consume
 - Whether to produce
 - Next Address
 - Next State
- ◆ **Depth ≥ 2 for full rate**




Shift Register Queue – Control

◆ State Empty

- ◆ If (i_v) then *consume*
- ◆ If ($!i_v$) then *idle*

◆ State Non-empty

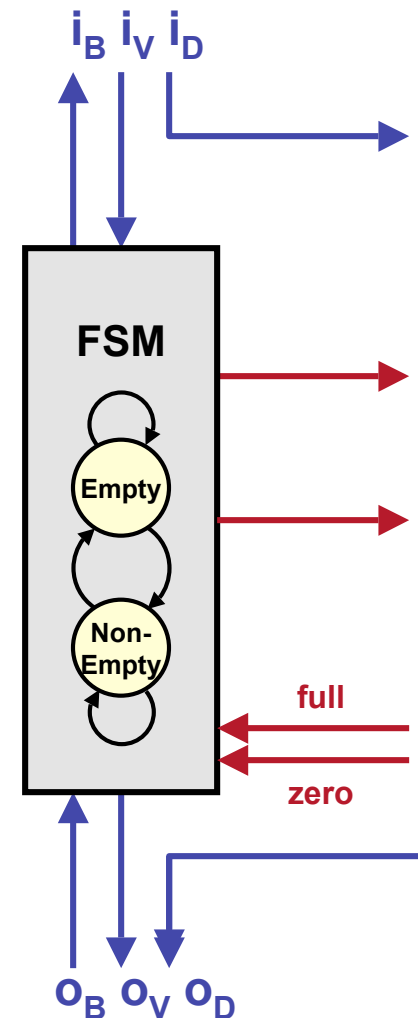- If (*full*) then
 - ◆ If (o_b) then *idle*
 - ◆ If ($!o_b$) then *produce*
- Else (*neither full nor empty*)
 - ◆ If ($i_v \wedge o_b$) then *consume*
 - ◆ If ($i_v \wedge !o_b$) then *consume* + *produce*
 - ◆ If ($!i_v \wedge o_b$) then *idle*
 - ◆ If ($!i_v \wedge !o_b$) then *produce*



Shift Register Queue – Verilog 1

```
module Q_srl (clock, reset, i_d, i_v, i_b, o_d, o_v, o_b);

    parameter depth = 16;        // - greatest #items in queue (2 <= depth <= 256)
    parameter width = 16;       // - width of data (i_d, o_d)

    input    clock;
    input    reset;

    input  [width-1:0] i_d;      // - input  stream data (concat data + eos)
    input                    i_v; // - input  stream valid
    output                   i_b; // - input  stream back-pressure

    output [width-1:0] o_d;     // - output stream data
    output                   o_v; // - output stream valid
    input                    o_b; // - output stream back-pressure
endmodule
```

Shift Register Queue – Verilog 2

```
parameter addrwidth =
    ( ((depth) ==0) ? 0 // - depth==0 LOG2=0
    : ((depth-1)>>0)==0) ? 0 // - depth<=1 LOG2=0
    : ((depth-1)>>1)==0) ? 1 // - depth<=2 LOG2=1
    : ((depth-1)>>2)==0) ? 2 // - depth<=4 LOG2=2
    : ((depth-1)>>3)==0) ? 3 // - depth<=8 LOG2=3
    : ((depth-1)>>4)==0) ? 4 // - depth<=16 LOG2=4
    : ((depth-1)>>5)==0) ? 5 // - depth<=32 LOG2=5
    : ((depth-1)>>6)==0) ? 6 // - depth<=64 LOG2=6
    : ((depth-1)>>7)==0) ? 7 // - depth<=128 LOG2=7
    : 8) // - depth<=256 LOG2=8
;

reg [addrwidth-1:0] addr, addr_, a_; // - SRL16 address
// for data output
reg shift_en_; // - SRL16 shift enable
reg [width-1:0] srl [depth-1:0]; // - SRL16 memory

parameter state_empty = 1'b0; // - state empty : o_v=0 o_d=UNDEFINED
parameter state_nonempty = 1'b1; // - state nonempty: o_v=1 o_d=srl[addr]
// #items in srl = addr+1

reg state, state_; // - state register
```

Shift Register Queue – Verilog 3

```
wire    addr_full_;           // - true iff addr==depth-1
wire    addr_zero_;          // - true iff addr==0

assign addr_full_ = (addr==depth-1);    // - queue full
assign addr_zero_ = (addr==0);         // - queue contains 1

assign o_d = srl[addr];               // - output data from queue
assign o_v = (state==state_empty) ? 0 : 1; // - output valid if non-empty
assign i_b = addr_full_;              // - input bp if full
```

Shift Register Queue – Verilog 4

```
always @(posedge clock or negedge reset) begin           // - seq always: FFs
    if (!reset) begin
        state <= state_empty;
        addr  <= 0;
    end
    else begin
        state <= state_;
        addr  <= addr_;
    end
end // always @ (posedge clock or negedge reset)

always @(posedge clock) begin                             // - seq always: SRL16
    // - infer enabled SRL16 from shifting srl array
    // - no reset capability; srl[] contents undefined on reset
    if (shift_en_) begin
        // synthesis loop_limit 256
        for (a_=depth-1; a_>0; a_=a_-1) begin
            srl[a_] <= srl[a_-1];
        end
        srl[0] <= i_d;
    end
end // always @ (posedge clock or negedge reset)
```

Shift Register Queue – Verilog 5

```
always @* begin                                // - combi always
  case (state)

    state_empty: begin                          // - (empty, will not produce)
      if (i_v) begin                            // - empty & i_v => consume
        shift_en_ <= 1;
        addr_     <= 0;
        state_    <= state_nonempty;
      end
    else begin                                  // - empty & !i_v => idle
      shift_en_ <= 0;
      addr_     <= 0;
      state_    <= state_empty;
    end
  end
end
```

Shift Register Queue – Verilog 6

```
state_nonempty: begin
    if (addr_full_) begin                // - (full, will not consume)
        if (o_b) begin                  // - full & o_b => idle
            shift_en_ <= 0;
            addr_      <= addr;
            state_     <= state_nonempty;
        end
    else begin                          // - full & !o_b => produce
        shift_en_ <= 0;
        addr_      <= addr-1;
        state_     <= state_nonempty;
    end
end
end
```

Shift Register Queue – Verilog 7

```
else begin
    // - (mid: neither empty nor full)
    if (i_v && o_b) begin // - mid & i_v & o_b => consume
        shift_en_ <= 1;
        addr_ <= addr+1;
        state_ <= state_nonempty;
    end
    else if (i_v && !o_b) begin // - mid & i_v & !o_b => cons+prod
        shift_en_ <= 1;
        addr_ <= addr;
        state_ <= state_nonempty;
    end
    else if (!i_v && o_b) begin // - mid & !i_v & o_b => idle
        shift_en_ <= 0;
        addr_ <= addr;
        state_ <= state_nonempty;
    end
    else if (!i_v && !o_b) begin // - mid & !i_v & !o_b => produce
        shift_en_ <= 0;
        addr_ <= addr_zero_ ? 0 : addr-1;
        state_ <= addr_zero_ ? state_empty : state_nonempty;
    end
end // else: !if(addr_full_)
end // case: state_nonempty
```

Shift Register Queue – Verilog 8


```
        endcase // case(state)
    end // always @ *

endmodule // Q_srl
```


Characterization on FPGA


- ◆ **Synplify Pro 8.0 compiler**
 - Options: 200MHz, 0.5ns outputs, FSM Explorer, FSM Compiler, Resource Sharing, Retiming, Pipelining
- ◆ **Target: Xilinx Spartan 3 1000 FPGA, speed -5**
 - XC3S1000 = 17,280 4-LUT cells
- ◆ **Script to compile with different depths, widths**
- ◆ **Graph in Excel using Pivot Charts**

SRL Queue: RTL (depth 16, width 16)

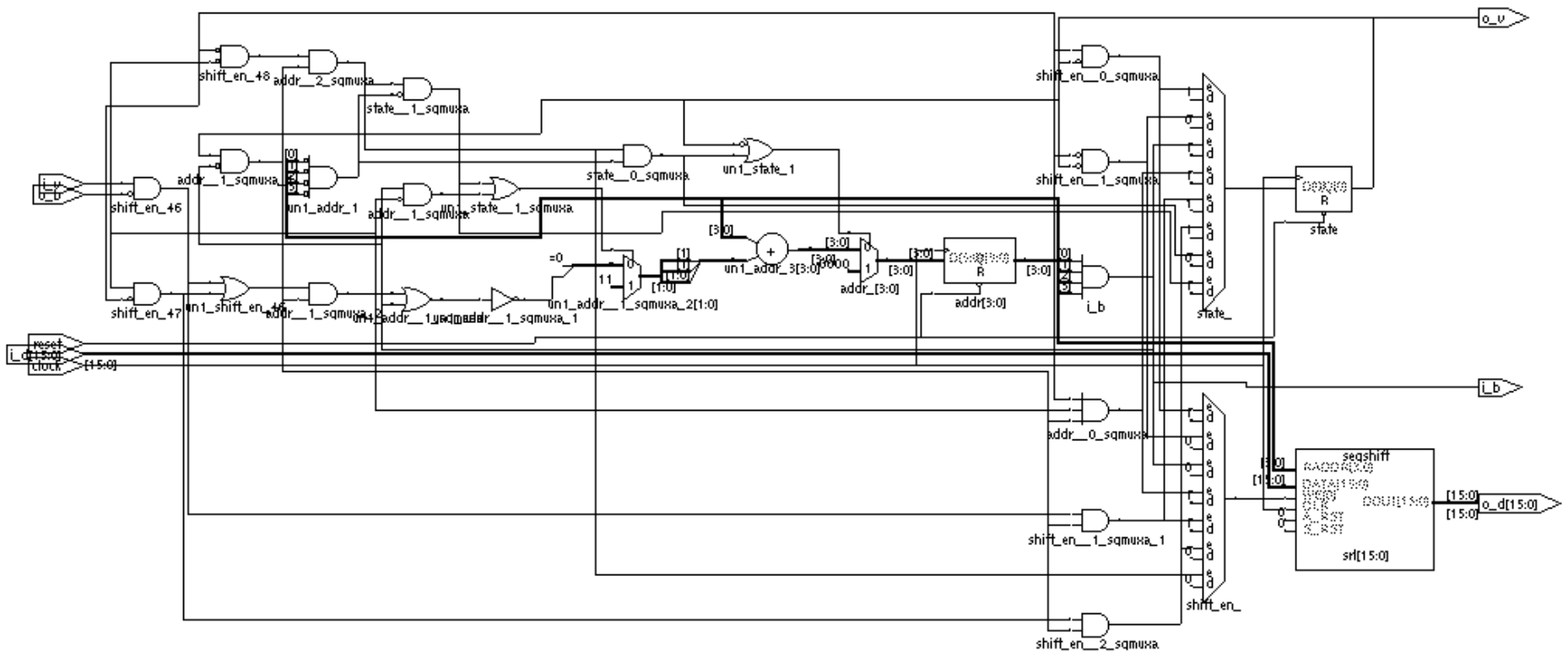

SRL Queue: Area


Revision Device

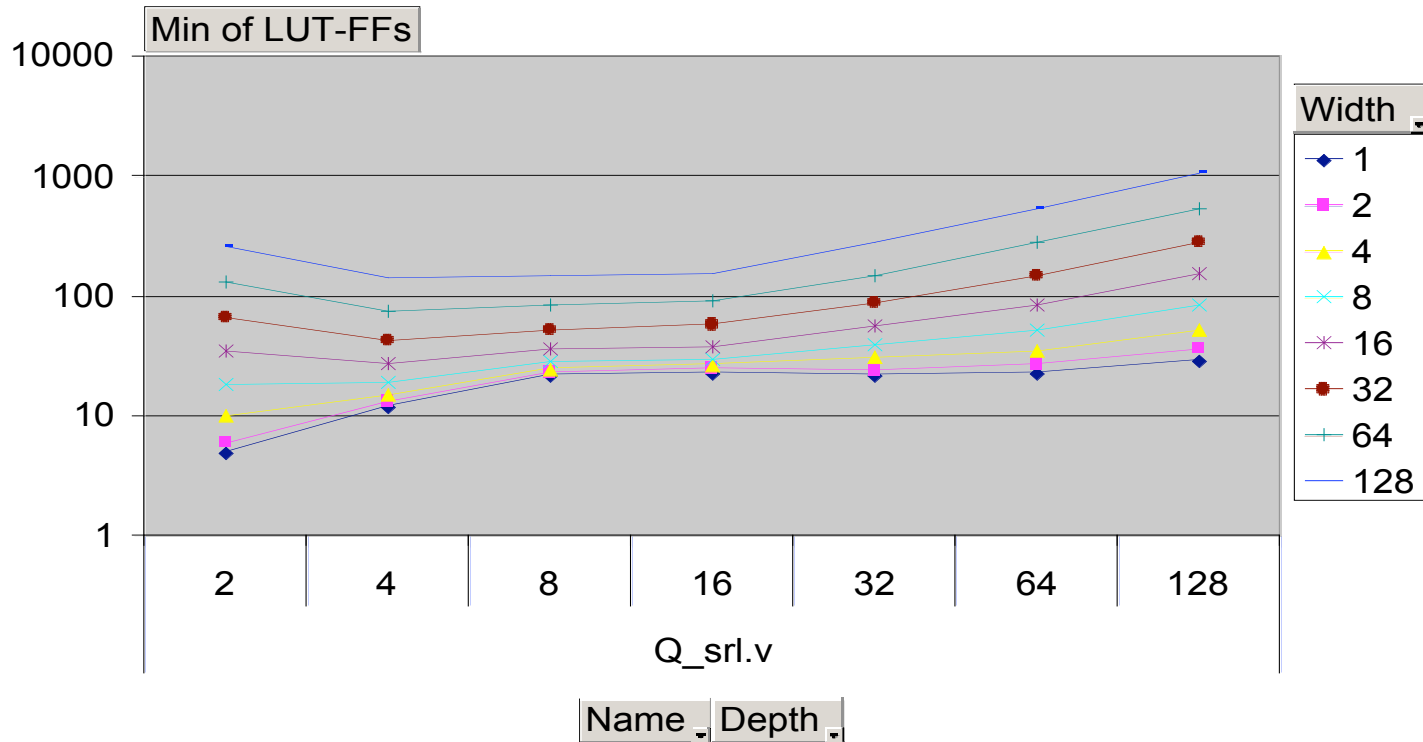

◆ **Depth 2: Shift register infers FFs, not SRL16**

SRL Queue: Area Per Bit


Revision rev_4__200mhz Device XC3S1000

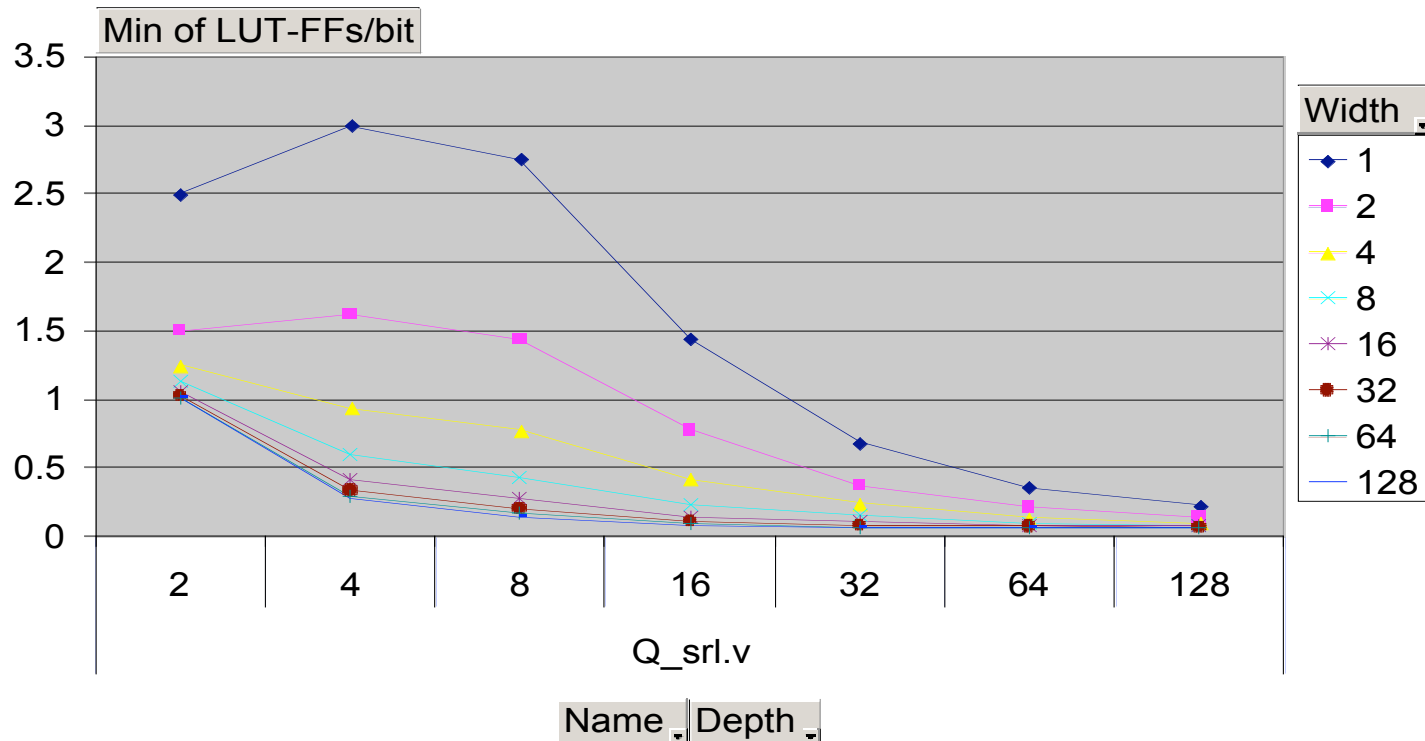

◆ Quickly beats enabled register queue (1 LUT-FF per bit)


SRL Queue: Speed

Revision Device

 

SRL Queue: Data Delay


Revision Device

 

- ◆ **Slow Clk-to-D due to dynamic addressing of shift register**

SRL Queue: Valid Delay


Revision Device

 

◆ **Clk-to-V = Clk-to-Q of state register**

SRL Queue: Back-Pressure Delay

 
Revision `rev_4__200mhz` Device `XC3S1000`



- ◆ **Clk-to-B slows due to (1) wider addr cmp, (2) higher addr fanout**


SRL Queue with Data Output Reg. (SRL+D)

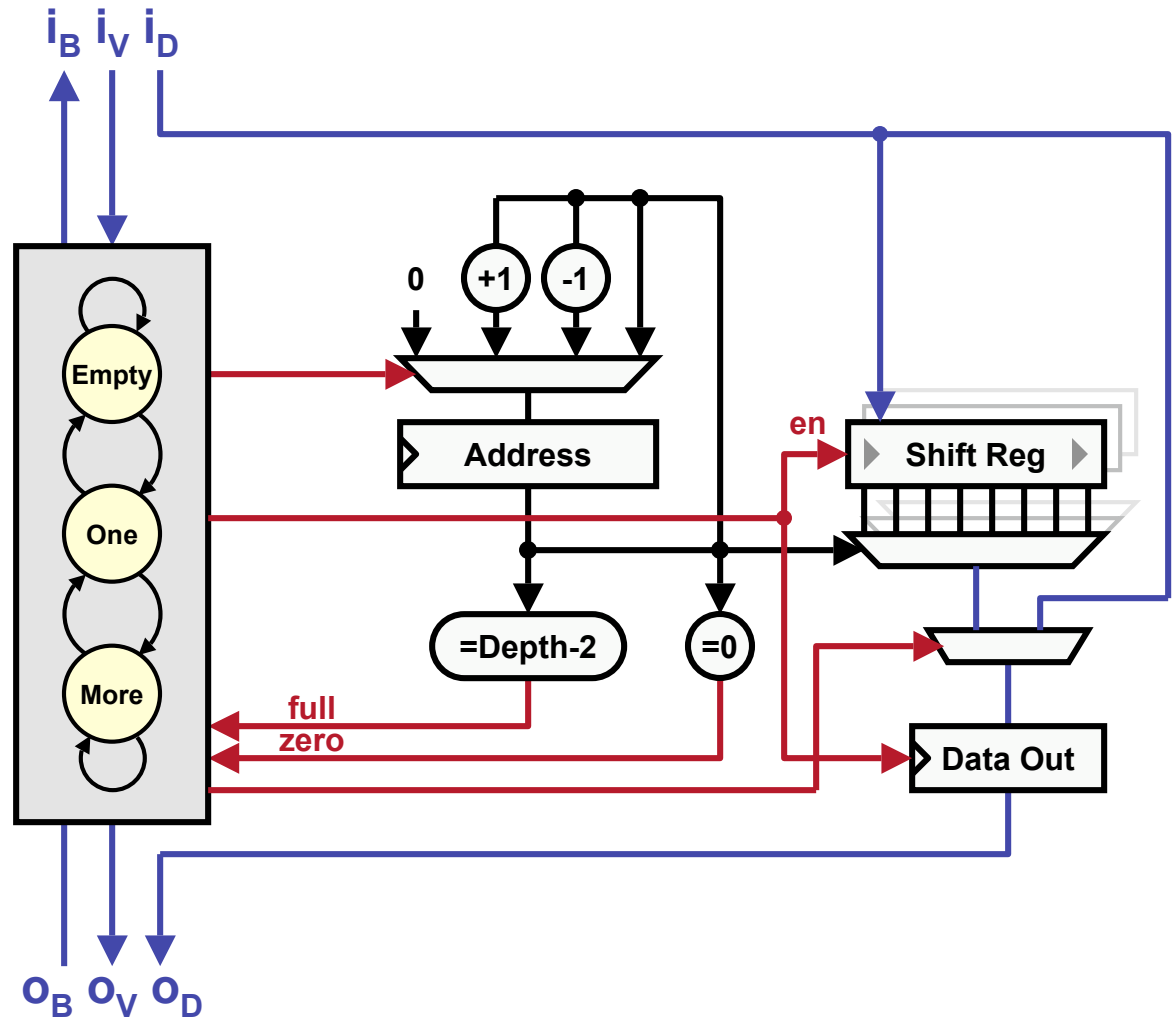- ◆ **Registered data out**
 - o_d (clock-to-Q delay)
 - Non-retimable
- ◆ **Data output register extends shift register**
- ◆ **Bypass shift register when queue empty**
- ◆ **3 States**
- ◆ **Address = number of stored elements minus 2**
- ◆ **Flow control**
 - $o_v = !(State == Empty)$
 - $i_b = (Address == Depth - 2)$




SRL+D Queue – Control

- ◆ **State Empty** (consume into D out reg.)
 - ◆ If (i_v) then *consume*
 - ◆ If ($!i_v$) then *idle*
- ◆ **State One** (consume into shift reg.)
 - ◆ If ($i_v \wedge o_b$) then *consume*
 - ◆ If ($i_v \wedge !o_b$) then *consume + produce*
 - ◆ If ($!i_v \wedge o_b$) then *idle*
 - ◆ If ($!i_v \wedge !o_b$) then *produce*
- ◆ **State More** (consume into shift reg.)
 - If (*full*) then
 - ◆ If (o_b) then *idle*
 - ◆ If ($!o_b$) then *produce*
 - Else (*neither full nor empty*)
 - ◆ If ($i_v \wedge o_b$) then *consume*
 - ◆ If ($i_v \wedge !o_b$) then *consume + produce*
 - ◆ If ($!i_v \wedge o_b$) then *idle*
 - ◆ If ($!i_v \wedge !o_b$) then *produce*

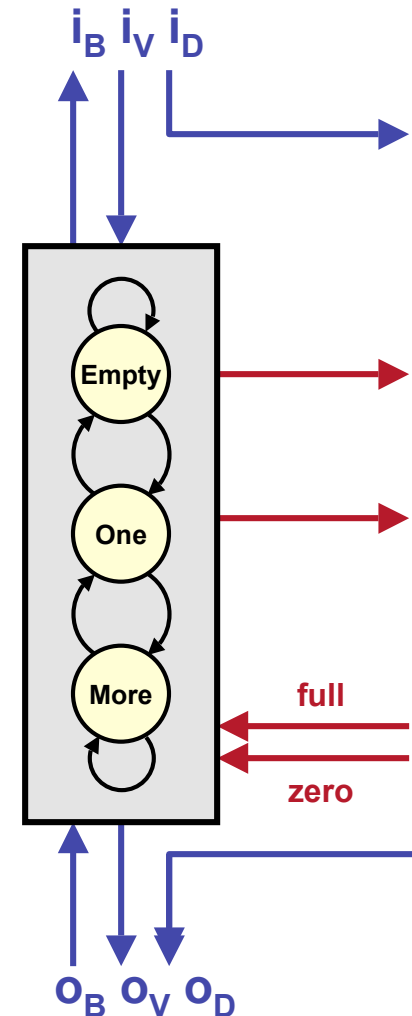

SRL+D: Data Delay


Revision Device

 

◆ **Clk-to-D = Clk-to-Q of data output register**

SRL+D Queue: Speedup


Revision Device

 

◆ Slight speedup, up to ~20%

SRL+D Queue: Area Change


Revision Device

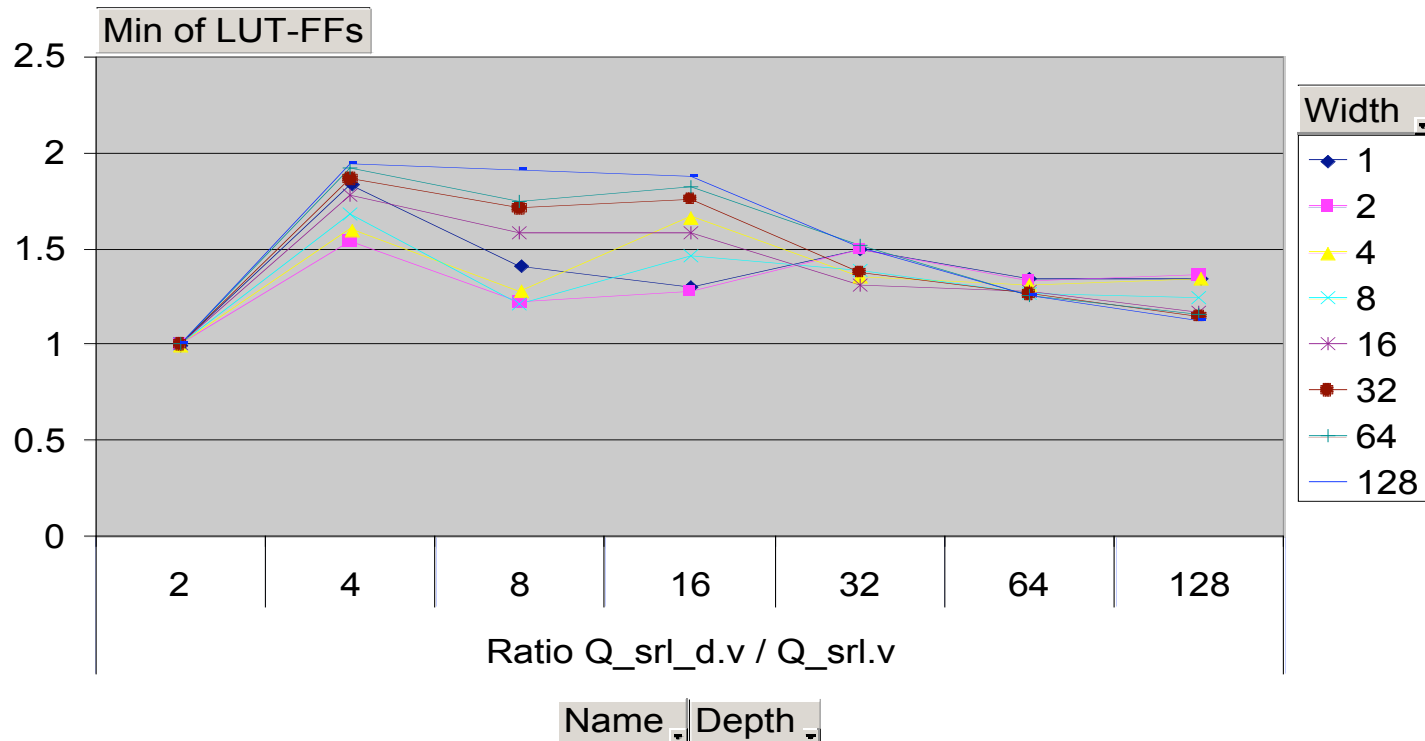

- ◆ Larger area from data out reg. – cannot pack with shift reg.

SRL+D Queue: Valid Delay

Revision Device

 

◆ $o_v = !(State==Empty)$, state is encoded


Pre-Computed Valid (SRL+DV)

◆ Registered valid out

- o_v (clock-to-Q delay)
- Non-retimable


◆ Flow control

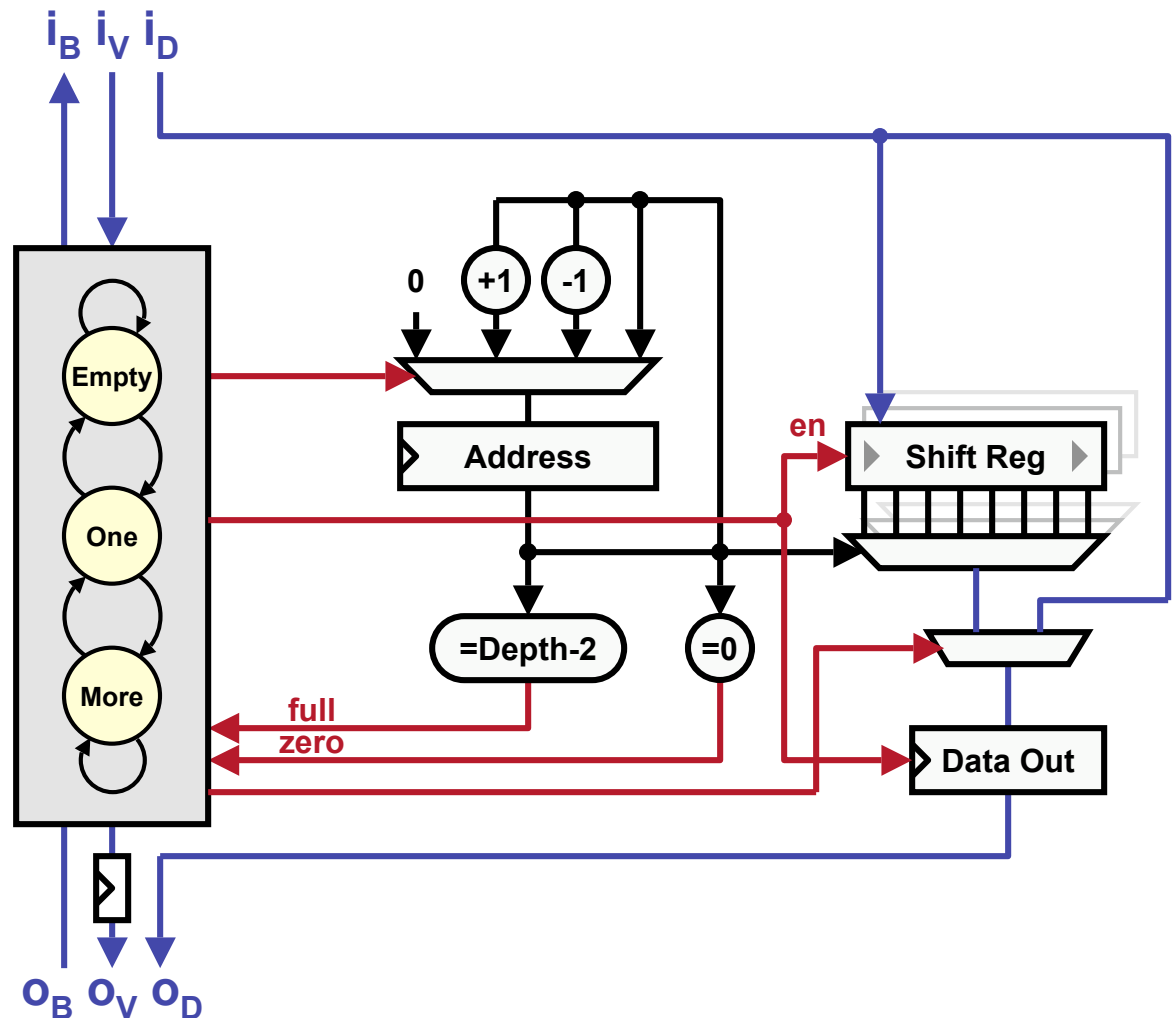- $o_{v_next} = !(State_next == Empty)$
- $i_b = (Address == Depth-2)$



SRL+DV: Valid Delay


Revision Device

 

◆ **Clk-to-V = Clk-to-Q of V output register**

SRL+DV: Back-Pressure Delay


Revision Device

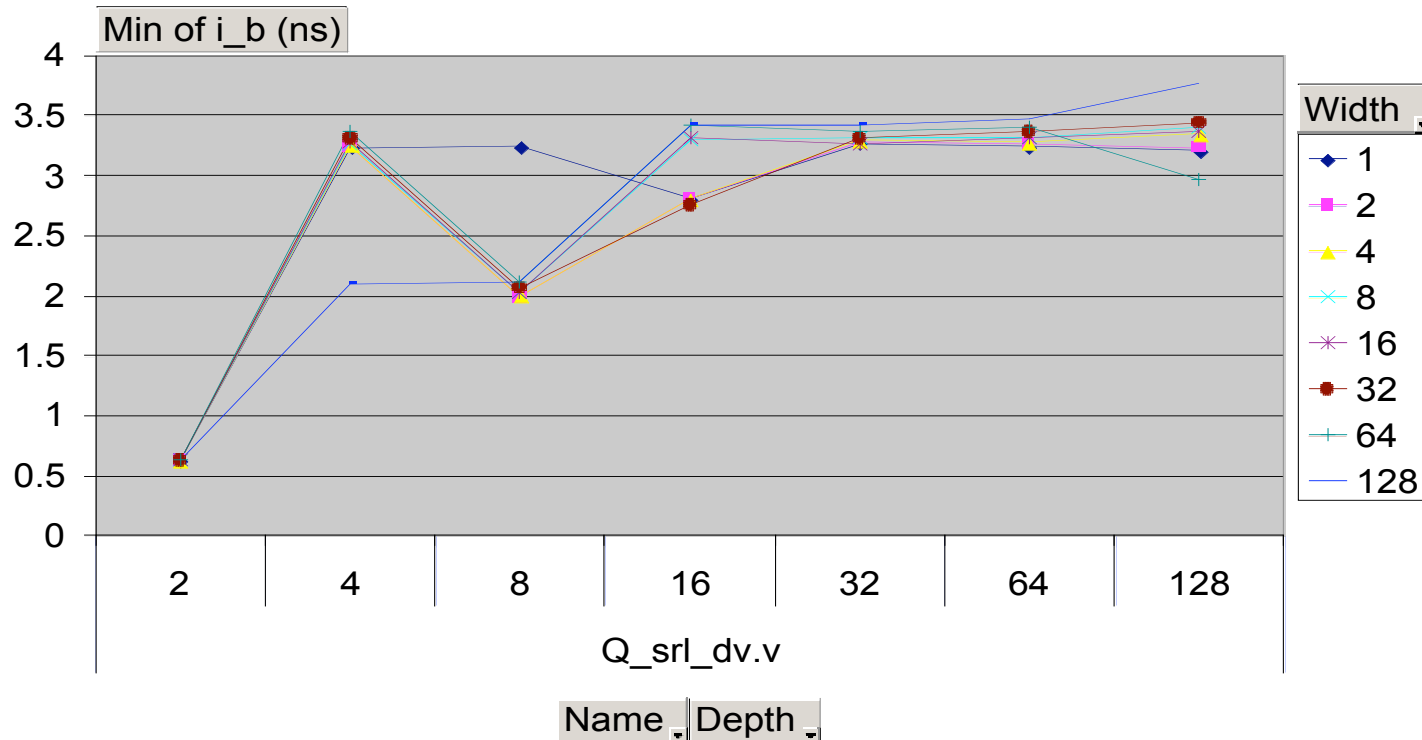

- ◆ Clk-to-B slows w/depth, (1) wider addr cmp, (2) higher addr fanout


Pre-Computed Back-Pressure (SRL+DVB)

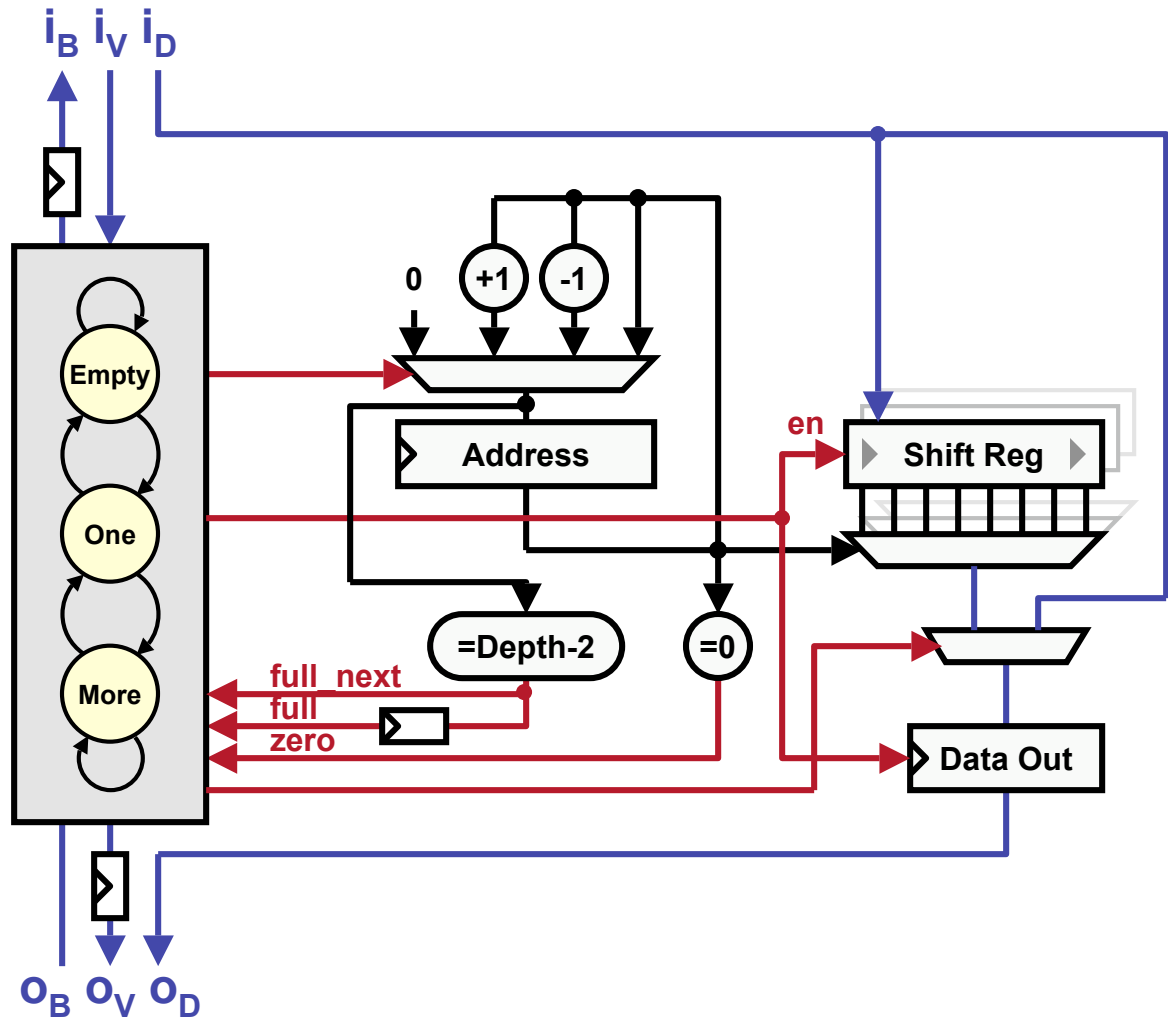- ◆ **Registered back-pressure out**
 - o_b (clock-to-Q delay)
 - Non-retimable
- ◆ **Based on pre-computed fullness**
 - $full_next = (Address_next == \overline{Depth-2})$
- ◆ **Flow control**
 - $o_v_next = !(State_next == Empty)$
 - $i_b_next = (Address_next == \overline{Depth-2})$



SRL+DVB: Back-Pressure Delay


Revision Device

 

◆ **Clk-to-B = Clk-to-Q of B output register**

SRL+DVB: Speed

Revision Device

 

◆ Can we improve speed?

4/8/05

Eylon Caspi

44

Specialized, Pre-Computed Fullness (SRL+DVBF)

◆ SRL+DVBF critical loop


{ full, FSM,
Address update,
Address compare }

◆ Speed up *full* pre-computation by special-casing *full_next* for each state

◆ Flow control


- $o_{v_next} = !(State_next == Empty)$
- $i_{b_next} = full_next$

◆ zero pre-computation is less critical

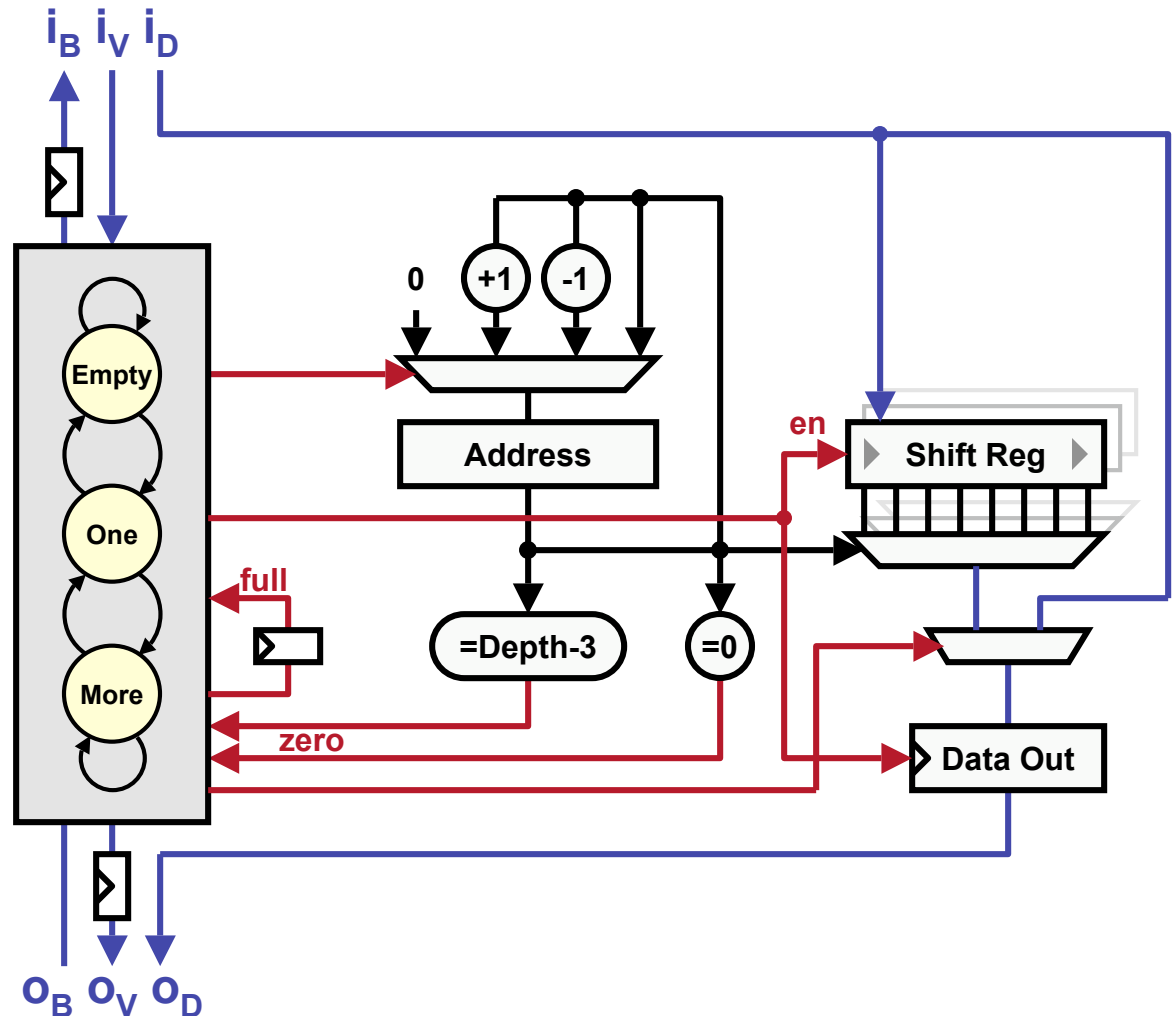

SRL+DVBF: Speedup


Revision Device

 

- ◆ Speedup from specialization of *full_next*, up to ~30%


SRL+DVBF: Speed

Revision Device

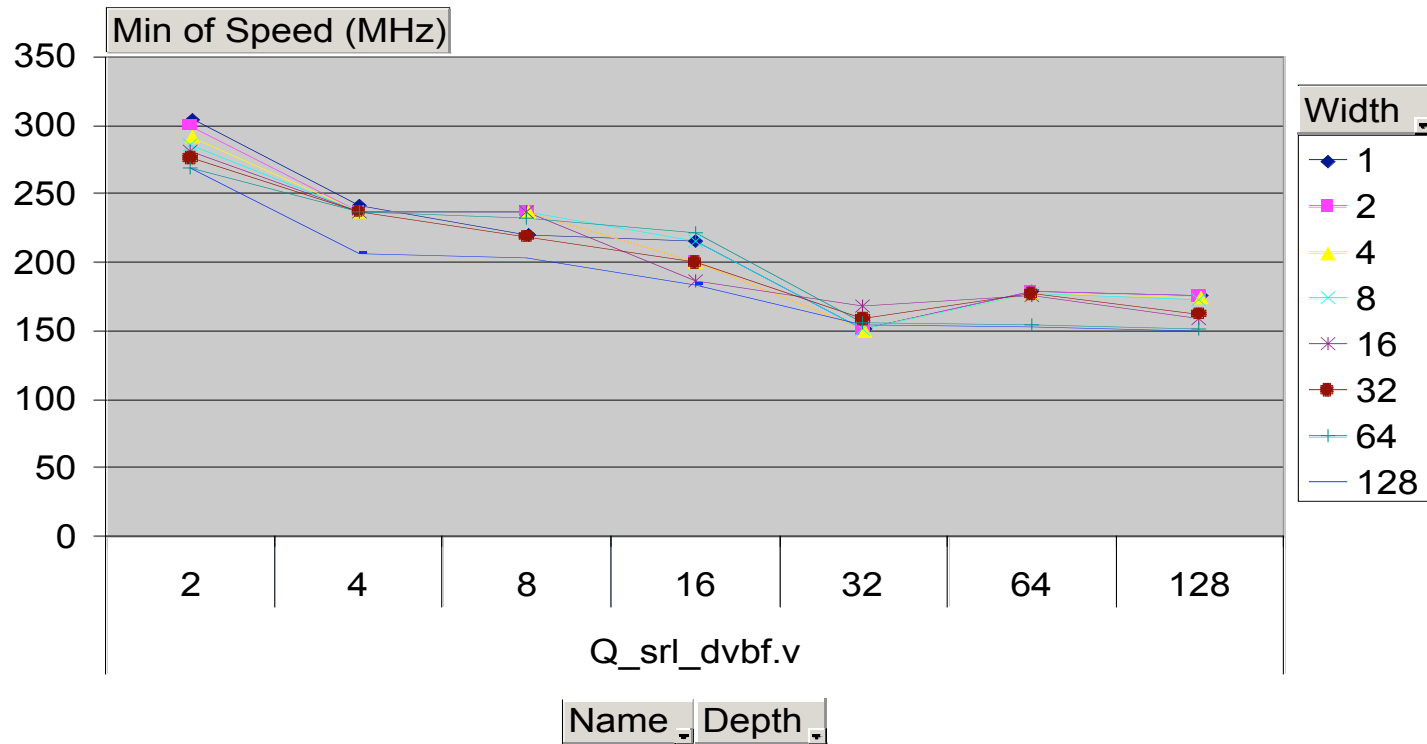

SRL+DVBF: Area Change


Revision Device

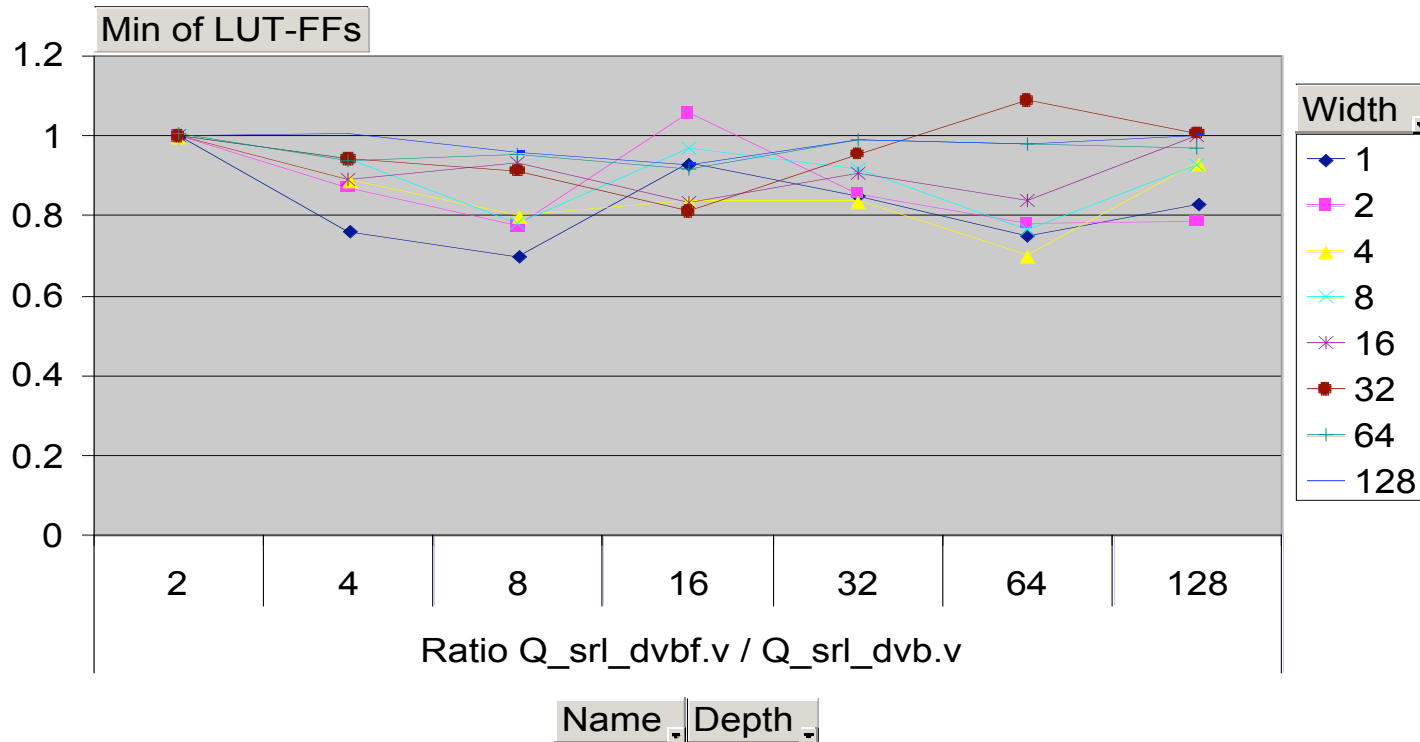

- ◆ Area savings from specialization of *full_next*, up to ~30%

SRL+DVBF: Area


Revision Device

 

Stream Enabled Pipelining

- ◆ **Pipelining = inserting registers to break-up long combinational delay, improve MHz**

 - Logic pipelining: break-up deep logic
- Interconnect pipelining: break-up long wires



- ◆ **Pipelining adds clock cycles of latency**

- Signals out of sync, stale

- ◆ **Requires architectural modification – *difficult***


- *E.g.* microprocessor pipelined function unit

- ◆ **Stream pipelining requires only *stream* modification – *easy***

- Stream abstraction (queue) admits arbitrary delay
- Stream implementation admits stylized pipelining


Interconnect Relaying

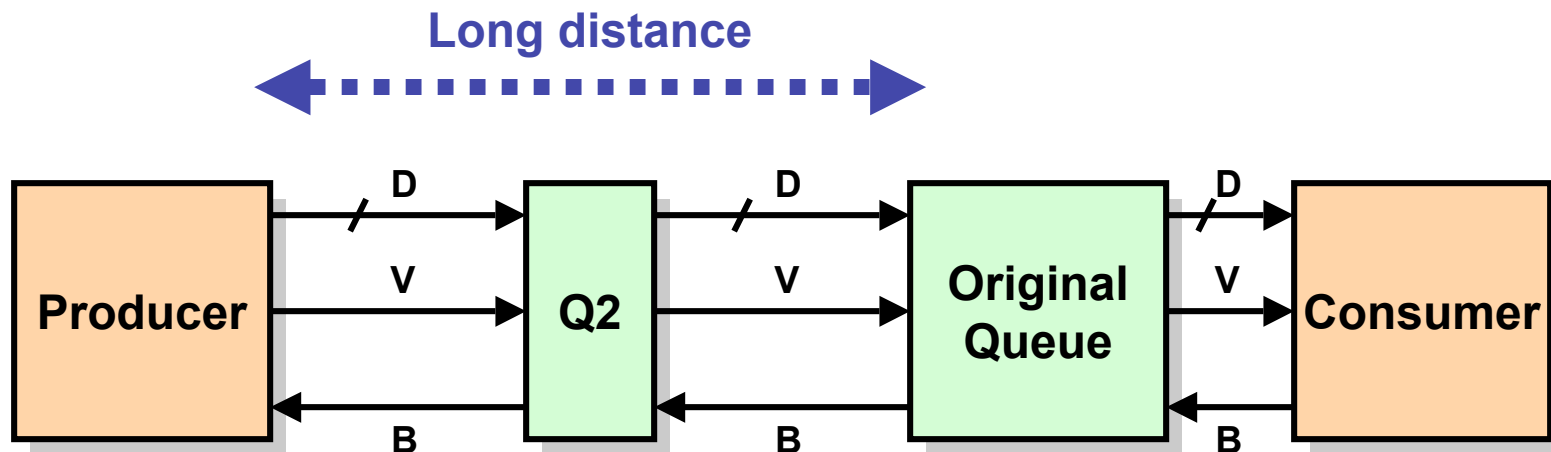- ◆ Break-up long distance streams
- ◆ Relay through depth-2 shift-register queue(s)
 - Need depth-2 for full throughput (depth-1 is 1/2 throughput)
 - Can cascade multiple relay stages for longer distance




Interconnect Pipelining

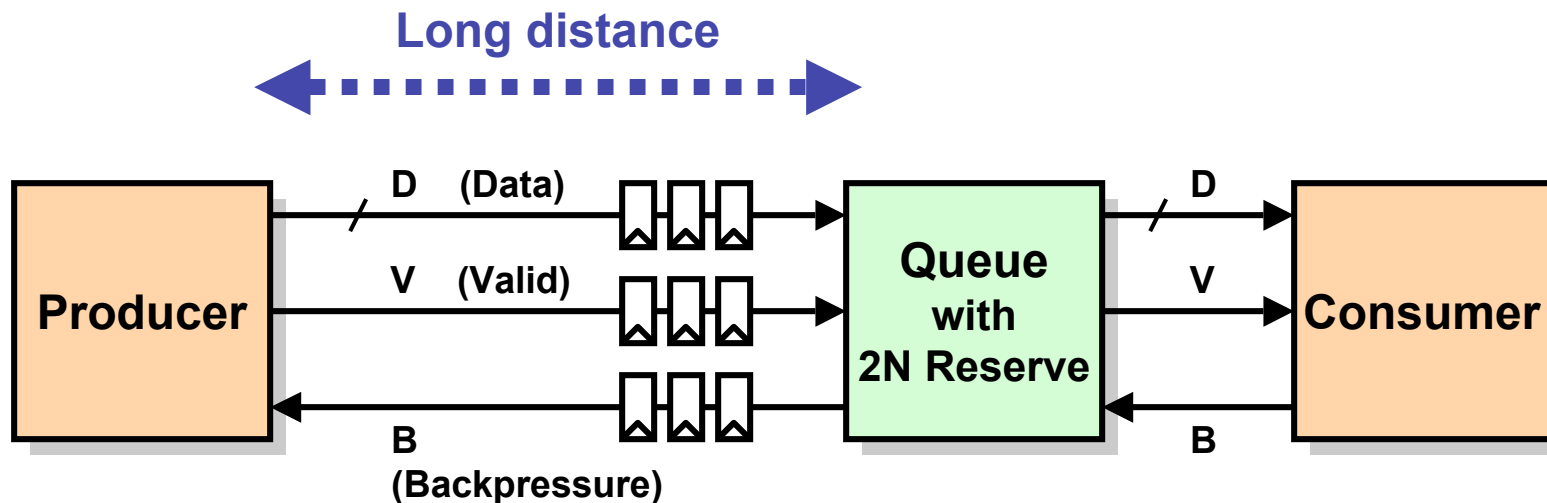- ◆ **Add N pipeline registers to D, V, B**
 - Mobile registers for placer
- ◆ **Stale flow control may overflow queue (by $2N$)**
 - Staleness = total delay on B-V feedback loop = $2N$
- ◆ **Modify downstream queue to emit back-pressure when empty slots $\leq 2N$**




Logic Pipelining

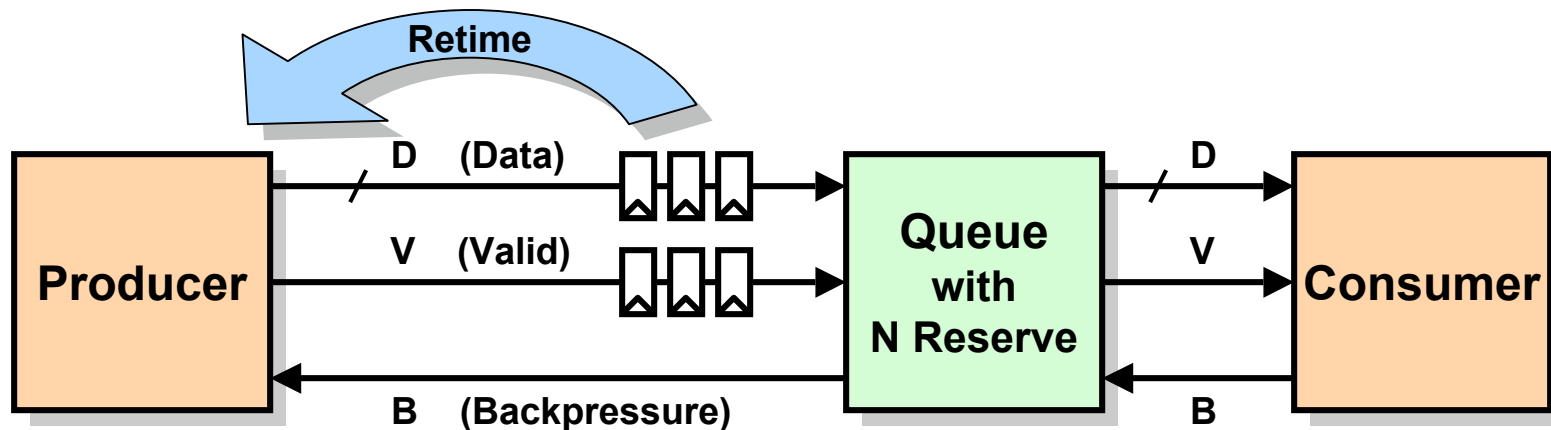- ◆ Add N pipeline registers to D , V
- ◆ Retime backwards
 - This pipelines feed-forward parts of producer's data-path
- ◆ Stale flow control may overflow queue (by N)
- ◆ Modify queue to emit back-pressure when empty slots $\leq N$
- ◆ No manual modification of processes!



Logic Relaying + Retiming

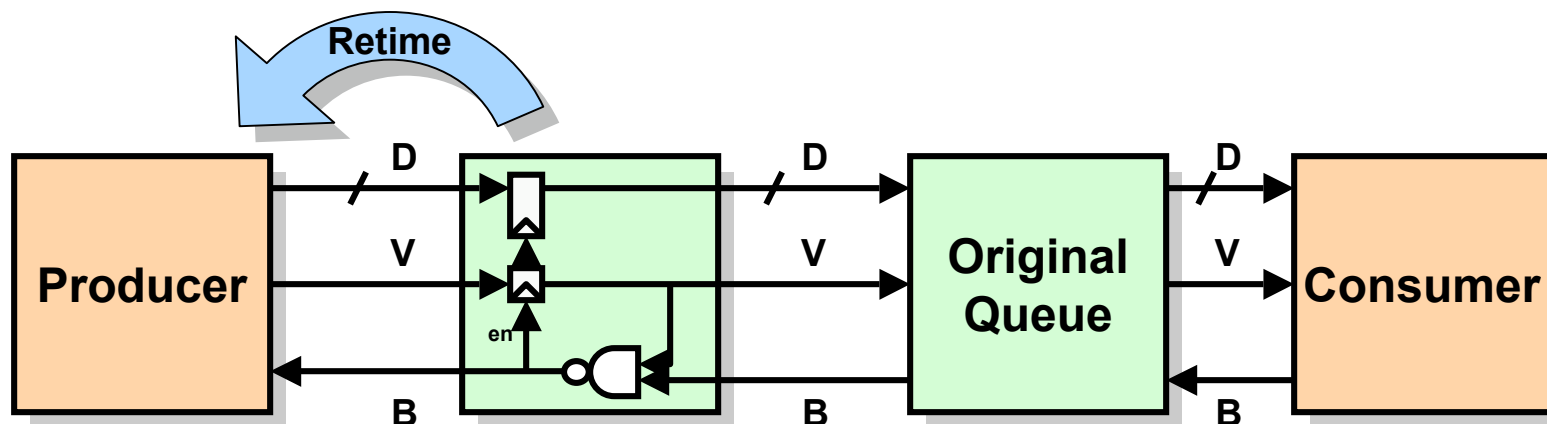- ◆ Break-up deep logic in a process
- ◆ Relay through enabled register queue(s)
- ◆ Retime registers into adjacent process
 - This pipelines feed-forward parts of process's datapath
 - Can retime into producer or consumer
- ◆ No manual modification of processes!



Summary

- ◆ **Queues reschedule data**
 - For performance, correctness, convenience
- ◆ **Queue Connected (Streaming) Systems**
 - Robust to delay, easy to pipeline
- ◆ **Queue Implementations**
 - Systolic – enabled register queue
 - Shift register queue + optimizations
- ◆ **Stream Enabled Pipelining**
 - Of interconnect, logic – without modifying process